

Op-Amp Circuit Analysis by Inspection

Eric Danson

May 25, 2025

The transfer function of a linear system can be represented in the general form

$$H(s) = H_0 \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2}) \cdots (1 + s/\omega_{z,m})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2}) \cdots (1 + s/\omega_{p,n})} \quad (1)$$

where the poles $\omega_{p1}, \omega_{p2}, \dots, \omega_{p,n}$ and zeros $\omega_{z1}, \omega_{z2}, \dots, \omega_{z,m}$ are roots of the denominator and numerator, the values for which the function goes to infinity and zero, respectively.

1 General Method

1. To find the poles, set the input (v_{in}) to zero, or to find the zeros, set the output (v_{out}) to zero.
2. Find the equivalent resistance, R_{eq} , seen by each independent capacitor, C_{ind} , in the input and feedback networks.
 - Capacitors in series ($C_1 \parallel C_2$) or in parallel ($C_1 + C_2$) are combined to form a single independent capacitor.
3. Calculate the pole and zero frequencies as $\omega_x = 1/(R_{eq}C_{ind})$.

2 Approximate Method

1. Series RC pairs in the input network form a pole, and pairs in the feedback network form a zero.
2. Parallel RC pairs in the input network form a zero, and pairs in the feedback network form a pole.
3. Calculate the pole and zero frequencies as $\omega_x = 1/(RC)$.

3 Examples

3.1 LEAD COMPENSATOR

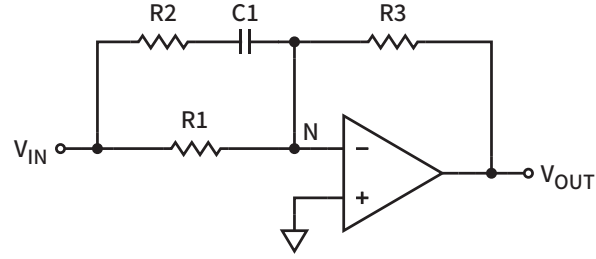


Fig. 1. Lead compensator schematic.

The DC gain for the inverting configuration is

$$H_0 = -R_3/R_1 \quad (2)$$

by considering C_1 as an open circuit (Fig. 1).

Obtain the poles by zeroing the input ($v_{in} = 0$) and finding the equivalent resistance seen by C_1 (Fig. 2(a)). Note that node N, the op-amp's negative input terminal, is a virtual ground.

$$\omega_p = 1/(R_2 C_1) \quad (3)$$

Likewise, obtain the zeros by zeroing the output ($v_{out} = 0$) (Fig. 2(b)).

$$\begin{aligned} \omega_z &= 1/[(R_1 + R_2) C_1] \\ &\approx 1/(R_1 C_1) \quad \text{for } R_1 \gg R_2 \end{aligned} \quad (4)$$

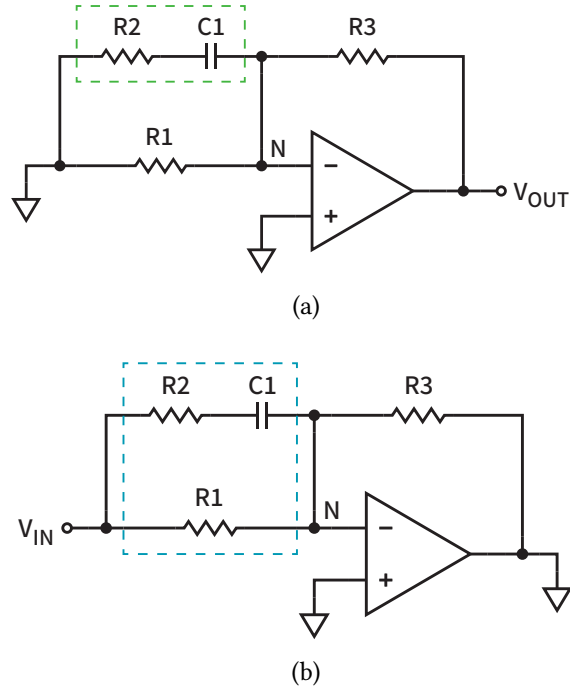


Fig. 2. Lead compensator equivalent circuit for finding (a) poles and (b) zeros.

The complete transfer function can be put in the form (Fig. 3)

$$\begin{aligned}
 H(s) &= H_0 \frac{1 + s/\omega_z}{1 + s/\omega_p} \\
 &= -\frac{R_3}{R_1} \cdot \frac{1 + s(R_1 + R_2)C_1}{1 + sR_2C_1} \\
 &\approx -\frac{R_3}{R_1} \cdot \frac{1 + sR_1C_1}{1 + sR_2C_1} \quad \text{for } R_1 \gg R_2.
 \end{aligned} \tag{5}$$

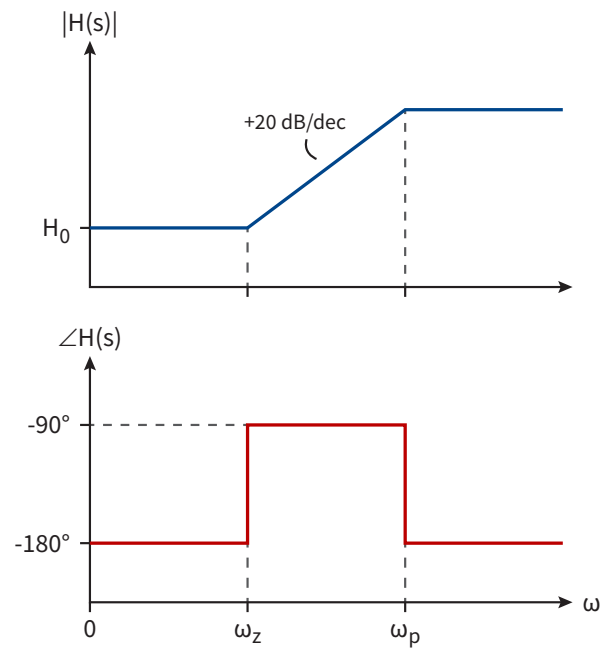


Fig. 3. Lead compensator Bode plot.

3.2 TYPE 2 COMPENSATOR

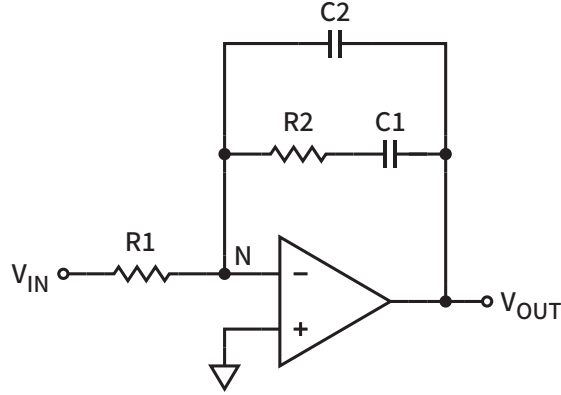


Fig. 4. Type 2 compensator schematic.

The DC gain formula for an inverting configuration is not valid here because the feedback impedance at DC is undefined. Instead, the constant value $H_0 = -1/(RC)$ in the integrator transfer function represents the gain at $\omega = 1 \text{ rad/s}$ and is determined by the input resistance and feedback capacitance (Fig. 4).


$$\begin{aligned} H_0 &= -1/[R_1(C_1 + C_2)] \\ &\approx -1/(R_1C_1) \quad \text{for } C_1 \gg C_2 \end{aligned} \quad (6)$$

Obtain the poles by zeroing the input ($v_{in} = 0$) and finding the equivalent resistance seen by C_1 and C_2 (Fig. 5(a)). Note that node N, the op-amp's negative input terminal, is a virtual ground.


$$\begin{aligned} \omega_p &= 1/[R_2(C_1 \parallel C_2)] \\ &\approx 1/(R_2C_2) \quad \text{for } C_1 \gg C_2 \end{aligned} \quad (7)$$

Likewise, obtain the zeros by zeroing the output ($v_{out} = 0$) (Fig. 5(b)).

$$\omega_z = 1/(R_2C_1) \quad (8)$$

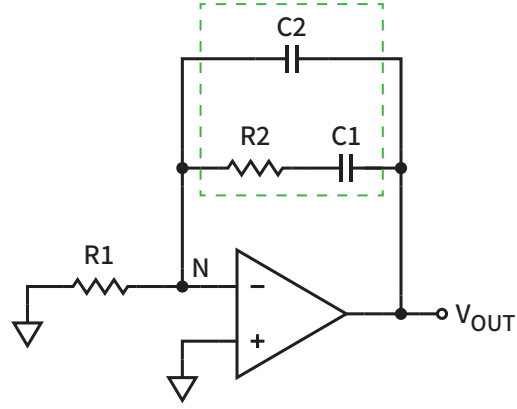

(a)

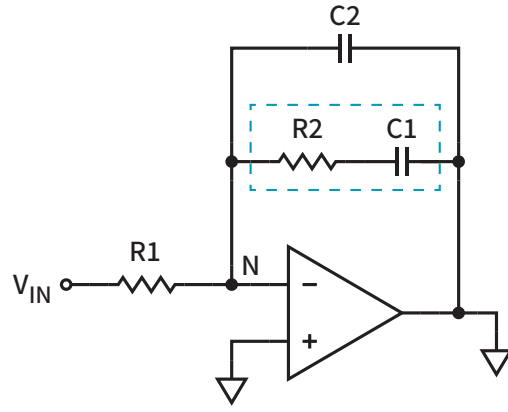

(b)

Fig. 5. Type 2 compensator equivalent circuit for finding (a) poles and (b) zeros.

The complete transfer function can be put in the form (Fig. 6)

$$\begin{aligned}
 H(s) &= H_0 \frac{1 + s/\omega_z}{s(1 + s/\omega_p)} \\
 &= -\frac{1}{R_1(C_1 + C_2)} \cdot \frac{1 + sR_2C_1}{s[1 + sR_2(C_1 \parallel C_2)]} \\
 &\approx -\frac{1}{R_1C_1} \cdot \frac{1 + sR_2C_1}{s(1 + sR_2C_2)} \quad \text{for } C_1 \gg C_2.
 \end{aligned} \tag{9}$$

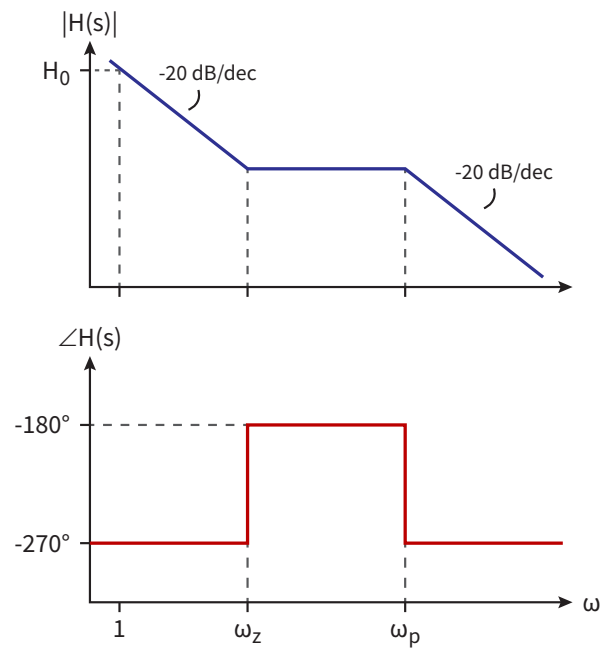


Fig. 6. Type 2 compensator Bode plot.

3.3 TYPE 3 COMPENSATOR

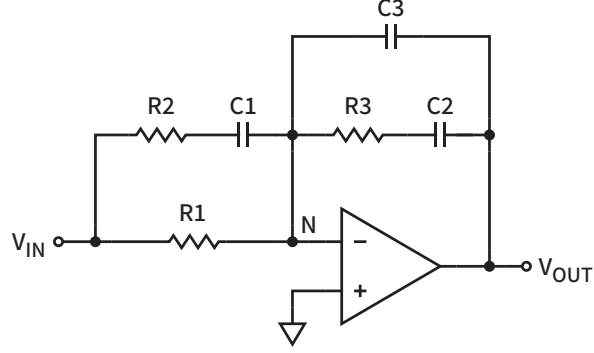


Fig. 7. Type 3 compensator schematic.

The DC gain formula for an inverting configuration is not valid here because the feedback impedance at DC is undefined. Instead, the constant value $H_0 = -1/(RC)$ in the integrator transfer function represents the gain at $\omega = 1 \text{ rad/s}$ and is determined by the input resistance and feedback capacitance (Fig. 7).

$$\begin{aligned} H_0 &= -1/[R_1(C_2 + C_3)] \\ &\approx -1/(R_1C_2) \quad \text{for } C_2 \gg C_3 \end{aligned} \quad (10)$$

Obtain the poles by zeroing the input ($v_{in} = 0$) and finding the equivalent resistances seen by C_1 , C_2 , and C_3 (Fig. 8(a)). Note that node N, the op-amp's negative input terminal, is a virtual ground.

$$\omega_{p1} = 1/(R_2C_1) \quad (11)$$

$$\begin{aligned} \omega_{p2} &= 1/[R_3(C_2 \parallel C_3)] \\ &\approx 1/(R_3C_3) \quad \text{for } C_2 \gg C_3 \end{aligned} \quad (12)$$

Likewise, obtain the zeros by zeroing the output ($v_{out} = 0$) (Fig. 8(b)).

$$\begin{aligned} \omega_{z1} &= 1/[(R_1 + R_2)C_1] \\ &\approx 1/(R_1C_1) \quad \text{for } R_1 \gg R_2 \end{aligned} \quad (13)$$

$$\omega_{z2} = 1/(R_3C_2) \quad (14)$$

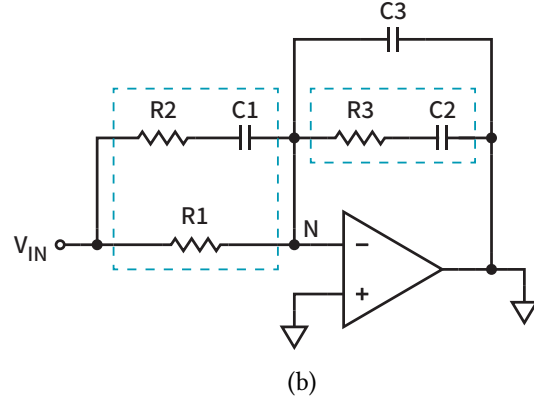
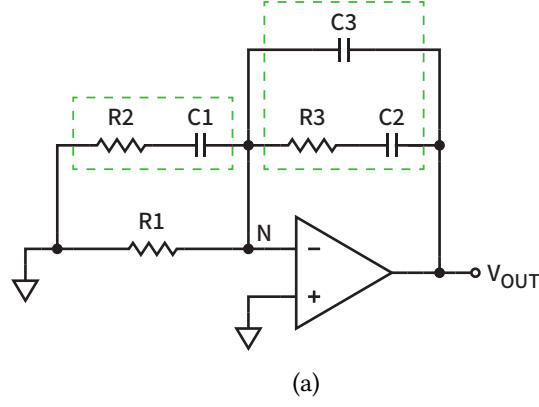


Fig. 8. Type 3 compensator equivalent circuit for finding (a) poles and (b) zeros.

The complete transfer function can be put in the form (Fig. 9)

$$\begin{aligned}
 H(s) &= H_0 \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2})}{s(1 + s/\omega_{p1})(1 + s/\omega_{p2})} \\
 &= -\frac{1}{R_1(C_2 + C_3)} \cdot \frac{[1 + s(R_1 + R_2)C_1](1 + sR_3C_2)}{s(1 + sR_2C_1)[1 + sR_3(C_2 \parallel C_3)]} \\
 &\approx -\frac{1}{R_1C_2} \cdot \frac{(1 + sR_1C_1)(1 + sR_3C_2)}{s(1 + sR_2C_1)(1 + sR_3C_3)} \quad \text{for } R_1 \gg R_2 \text{ and } C_2 \gg C_3.
 \end{aligned} \tag{15}$$

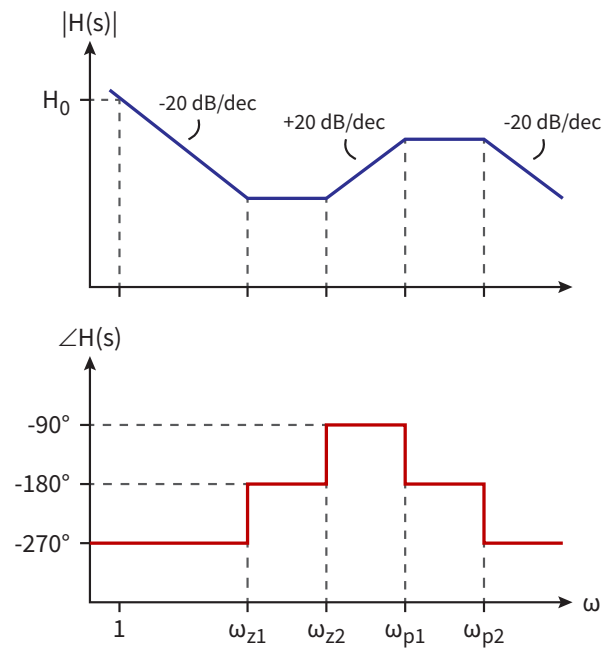


Fig. 9. Type 3 compensator Bode plot.

4 Appendix

4.1 LEAD COMPENSATOR TRANSFER FUNCTION DERIVATION

$$Z_f = R_3 \quad (16)$$

$$\begin{aligned} Z_i &= R_1 \parallel \left(R_2 + \frac{1}{sC_1} \right) \\ &= \frac{R_1 \left(R_2 + \frac{1}{sC_1} \right)}{R_1 + R_2 + \frac{1}{sC_1}} \\ &= \frac{R_1 + sR_1R_2C_1}{1 + s(R_1 + R_2)C_1} \end{aligned} \quad (17)$$

$$\begin{aligned} H(s) &= -\frac{Z_f}{Z_i} \\ &= -R_3 \cdot \frac{1 + s(R_1 + R_2)C_1}{R_1 + sR_1R_2C_1} \\ &= -\frac{R_3}{R_1} \cdot \frac{1 + s(R_1 + R_2)C_1}{1 + sR_2C_1} \\ &= H_0 \frac{1 + s/\omega_z}{1 + s/\omega_p} \end{aligned} \quad (18)$$

$$H_0 = -\frac{R_3}{R_1} \quad (19)$$

$$\omega_p = \frac{1}{R_2C_1} \quad (20)$$

$$\omega_z = \frac{1}{(R_1 + R_2)C_1} \quad (21)$$

4.2 TYPE 2 COMPENSATOR TRANSFER FUNCTION DERIVATION

$$\begin{aligned}
 Z_f &= \left(R_2 + \frac{1}{sC_1} \right) \parallel \frac{1}{sC_2} \\
 &= \frac{\left(R_2 + \frac{1}{sC_1} \right) \frac{1}{sC_2}}{R_2 + \frac{1}{sC_1} + \frac{1}{sC_2}} \\
 &= \frac{1 + sR_2C_1}{s(C_1 + C_2 + sR_2C_1C_2)}
 \end{aligned} \tag{22}$$

$$Z_i = R_1 \tag{23}$$

$$\begin{aligned}
 H(s) &= -\frac{Z_f}{Z_i} \\
 &= -\frac{1 + sR_2C_1}{s(C_1 + C_2 + sR_2C_1C_2)} \cdot \frac{1}{R_1} \\
 &= -\frac{1}{R_1(C_1 + C_2)} \cdot \frac{1 + sR_2C_1}{s\left(1 + \frac{sR_2C_1C_2}{C_1 + C_2}\right)} \\
 &= -\frac{1}{R_1(C_1 + C_2)} \cdot \frac{1 + sR_2C_1}{s[1 + sR_2(C_1 \parallel C_2)]} \\
 &= H_0 \frac{1 + s/\omega_z}{s(1 + s/\omega_p)}
 \end{aligned} \tag{24}$$

$$H_0 = -\frac{1}{R_1(C_1 + C_2)} \tag{25}$$

$$\omega_p = \frac{1}{R_2(C_1 \parallel C_2)} \tag{26}$$

$$\omega_z = \frac{1}{R_2C_1} \tag{27}$$

4.3 TYPE 3 COMPENSATOR TRANSFER FUNCTION DERIVATION

$$\begin{aligned}
 Z_f &= \left(R_3 + \frac{1}{sC_2} \right) \parallel \frac{1}{sC_3} \\
 &= \frac{\left(R_3 + \frac{1}{sC_2} \right) \frac{1}{sC_3}}{R_3 + \frac{1}{sC_2} + \frac{1}{sC_3}} \\
 &= \frac{1 + sR_3C_2}{s(C_2 + C_3 + sR_3C_2C_3)}
 \end{aligned} \tag{28}$$

$$\begin{aligned}
 Z_i &= R_1 \parallel \left(R_2 + \frac{1}{sC_1} \right) \\
 &= \frac{R_1 \left(R_2 + \frac{1}{sC_1} \right)}{R_1 + R_2 + \frac{1}{sC_1}} \\
 &= \frac{R_1 + sR_1R_2C_1}{1 + s(R_1 + R_2)C_1}
 \end{aligned} \tag{29}$$

$$\begin{aligned}
 H(s) &= -\frac{Z_f}{Z_i} \\
 &= -\frac{1 + sR_3C_2}{s(C_2 + C_3 + sR_3C_2C_3)} \cdot \frac{1 + s(R_1 + R_2)C_1}{R_1 + sR_1R_2C_1} \\
 &= -\frac{1}{R_1(C_2 + C_3)} \cdot \frac{(1 + sR_3C_2)[1 + s(R_1 + R_2)C_1]}{s\left(1 + \frac{R_3C_2C_3}{C_2 + C_3}\right)(1 + sR_2C_1)} \\
 &= -\frac{1}{R_1(C_2 + C_3)} \cdot \frac{[1 + s(R_1 + R_2)C_1](1 + sR_3C_2)}{s(1 + sR_2C_1)[1 + sR_3(C_2 \parallel C_3)]} \\
 &= H_0 \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2})}{s(1 + s/\omega_{p1})(1 + s/\omega_{p2})}
 \end{aligned} \tag{30}$$

$$H_0 = -\frac{1}{R_1 (C_2 + C_3)} \quad (31)$$

$$\omega_{p1} = \frac{1}{R_2 C_1} \quad (32)$$

$$\omega_{p2} = \frac{1}{R_3 (C_2 \parallel C_3)} \quad (33)$$

$$\omega_{z1} = \frac{1}{(R_1 + R_2) C_1} \quad (34)$$

$$\omega_{z2} = \frac{1}{R_3 C_2} \quad (35)$$